

# Tutorial 5 Questions

Nan Meng

University of Hong Kong

*u3003637@connect.hku.hk*

March 3, 2016

# Overview

- \* **Learning Objectives:**

Analyze circuits with ideal operational amplifiers

- \* **Basics**

- Symbols & Rules
- Operational Amplifiers
  - The Ideal op-amp Model
  - Ideal op-amp in a negative feedback configuration

- \* **Questions & Summary**

# Symbols & Rules(Recap)

- Operational Amplifiers

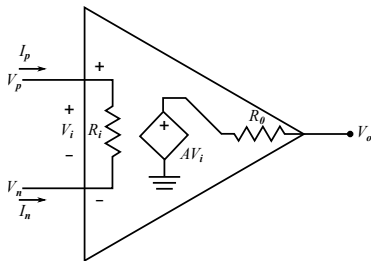


Figure : Equivalent circuit model of op-amp device

In the absence of any load at the output, the output voltage is

$$V_o = AV_i = A(V_p - V_n)$$

# Operational Amplifiers(Recap)

- **Operational Amplifiers**

In the absence of any load at the output, the output voltage is

$$V_o = AV_i = A(V_p - V_n)$$

Which indicates that the output voltage  $V_o$  is a function of the difference between the input voltages  $V_p$  and  $V_n$ . For this reason op-amps are **difference amplifiers**.

# Operational Amplifiers(Recap)

- The Ideal Op-amp Model

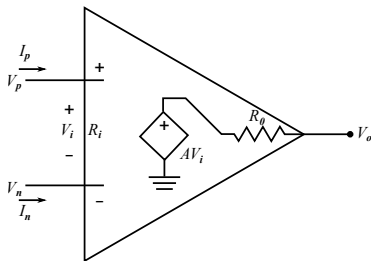


Figure : Ideal op-amp model

# Operational Amplifiers(Recap)

An ideal op-amp is a device which acts as an ideal voltage controlled voltage source. Referring to Figure in the previous slide, this implies that the device will have the following characteristics:

- \* **No current flows into the input terminals** of the device. This is equivalent to having an infinite input resistance  $R_i = \infty$ . In practical terms this implies that the amplifier device will make no power demands on the input signal source.
- \* **Have a zero output resistance ( $R_o = 0$ )**. This implies that the output voltage is independent of the load connected to the output.

# Operational Amplifiers(Recap)

## • The Ideal Op-amp Model

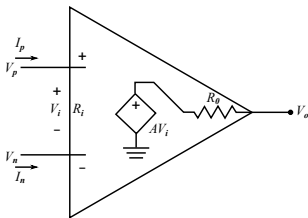


Figure : Ideal op-amp model

\* In summary, the ideal op-amp conditions are:

- $I_p = I_n = 0$  No current into the input terminals
- $R_i \rightarrow \infty$  Infinite input resistance
- $R_o = 0$  Zero output resistance
- $A \rightarrow \infty$  Infinite open loop gain

# Operational Amplifiers(Recap)

- When an op-amp is arranged with a **negative feedback** the ideal rules are:
  - \*  $I_p = I_n = 0$ : input current constraint
  - \*  $V_n = V_p$ : input voltage constraint


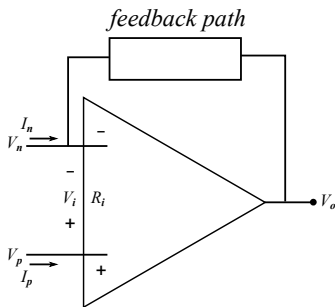


Figure : Basic negative feedback configuration.

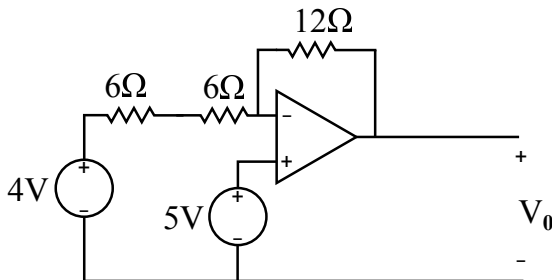


## Question 1

- \* Determine  $V_0$  in the following circuit. Assume that the op-amp is ideal.



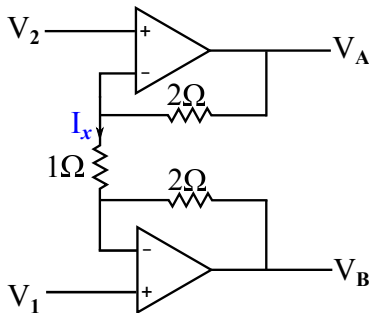
## Question 2

- \* Determine the current  $I_x$  when  $V_1 = 1V$  and  $V_2 = 2V$ .
- \* Determine the voltage  $V_A$  when  $V_1 = 1V$  and  $V_2 = 2V$ .
- \* Determine a general expression for  $V_A$  in terms of  $V_1$  and  $V_2$ .



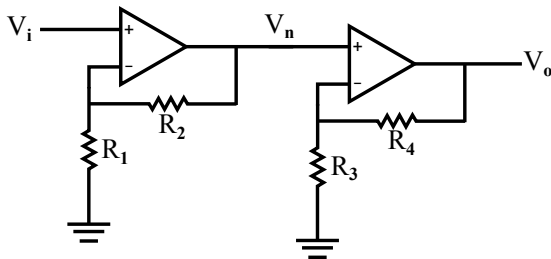
## Question 3

- \* Use a single op-amp and resistors to make a circuit that is equivalent to the following circuit.



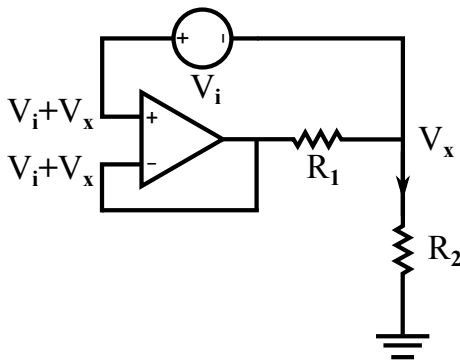
## Question 4

- \* Use the ideal op-amp model ( $V_+ = V_-$ ) to determine an expression for the output current  $I_0$  in terms of the input voltage  $V_i$  and resistors  $R_1$  and  $R_2$ .


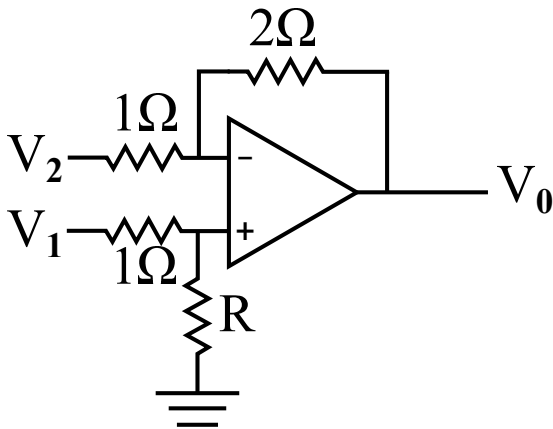
## Question 5


- \* Determine  $R$  so that  $V_0 = 2(V_1 - V_2)$ .


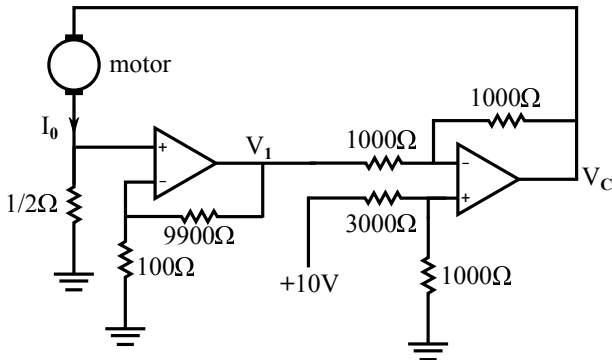
## Question 6


- \* A proportional controller that regulates the current through a motor by setting the motor voltage  $V_C$  to  $V_C = K(I_d - I_0)$

- \*  $K$  is the gain(ohms)
- \*  $I_d$  is the desired motor current
- \*  $I_0$  is the actual current through the motor.



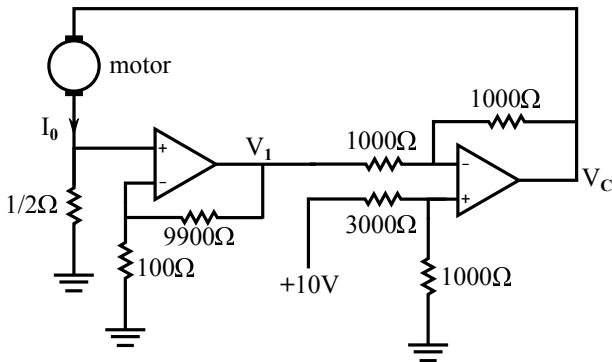
## Question 6

- \* A proportional controller that regulates the current through a motor by setting the motor voltage  $V_C$  to  $V_C = K(I_d - I_0)$
- \* Consider the circuit inside the dotted rectangle. Determine  $V_1$  as a function of  $I_0$
- \* Determine the gain  $K$  and desired motor current  $I_d$


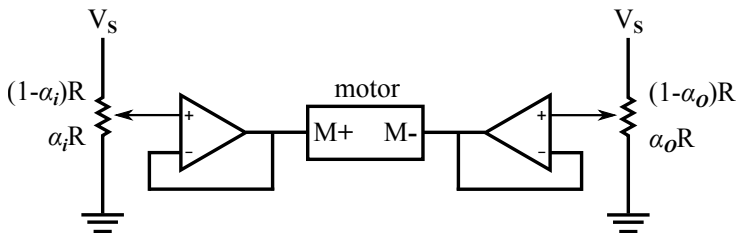
## Question 7


- \* The shaft angle of the output pot tracks that of the input pot
  - \* If the person turn the left potentiometer (the input pot), then the motor will turn the right potentiometer (the output pot)





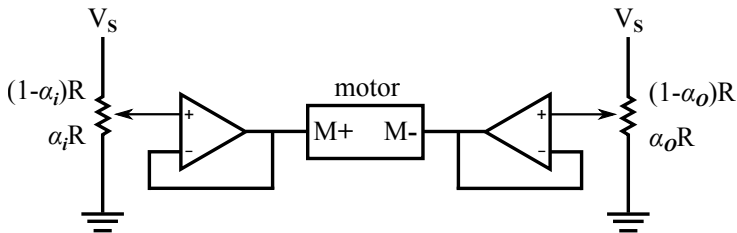
## Question 7

- \* Pot resistances depends on shaft angle
  - \* Lower part of the pot is  $\alpha R$
  - \* Upper part is  $(1 - \alpha)R$ , where  $R = 1000\Omega$
  - \*  $\alpha$  is from 0 (most counterclockwise position) to 1 (most clockwise position)
- \* If  $\alpha_i = \alpha_o$ , then the voltage to the motor ( $V_{M+} - V_{M-}$ ) is positive, and the motor turns clockwise (so as to increase  $\alpha_o$ ) – i.e., **positive motor voltage clockwise rotation**



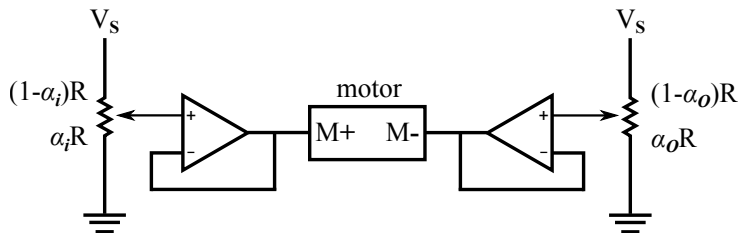
## Question 7

- \* Determine an expression for  $V_{M+}$  in terms of  $\alpha_i$ ,  $R$ , and  $V_s$ .



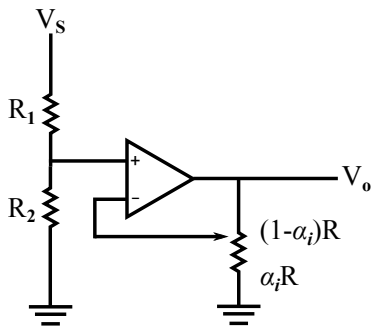
## Question 7

- \* The following circuit produces a voltage  $V_o$  that depends on the position of the input pot. Determine an expression for the voltage  $V_o$  in terms of  $\alpha_i$ ,  $R$ ,  $R_1$ ,  $R_2$ , and  $V_s$ .



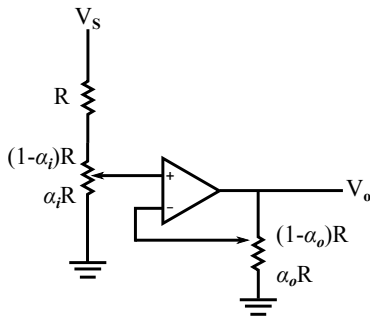
## Question 7

- \* The following circuit produces a voltage  $V_o$  that depends on the positions of both pots. Determine an expression for  $V_o$  in terms of  $\alpha_i$ ,  $\alpha_o$ ,  $R$ , and  $V_s$


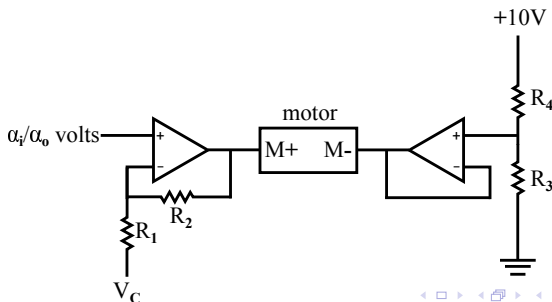
## Question 7


- \* Assume that we are provided with a circuit whose output is  $\alpha_i/\alpha_o$  volts. We want to design a motor controller of the following form so that the motor shaft angle (which is proportional to  $\alpha_o$ ) will track the input pot angle (which is proportional to  $\alpha_i$ ).
- \* Assume that  $R_1 = R_3 = R_4 = 1000\Omega$  and  $V_c = 0$ . Is it possible to choose  $R_2$  so that  $\alpha_o$  tracks  $\alpha_i$ ? If **yes**, enter an acceptable value for  $R_2$


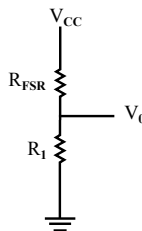
## Question 8


- \* You have to design a hammer machine(i.e. using a hammer to hit a platform to see how strong the participants are). The design goal is to generate an output voltage ( $V_o$ ) which is proportional to the force( $F$ ) applied on the hammer, i.e.  $V_o = m \times F + C$  ( $m > 0$  and  $C > 0$ ).
- \* (a) You found a force-sensitive resistor (FSR) from the catalog, which can be modeled by  $R_{FSR} = 10k\Omega/F$

- \* You then design a circuit as a potential divider. Will this circuit correctly implement?



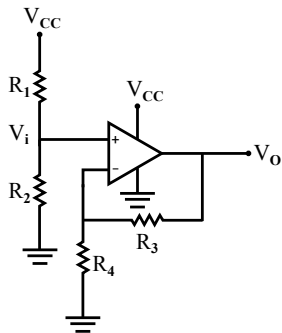
## Question 8

- \* (b) Find the gain of the following circuit:


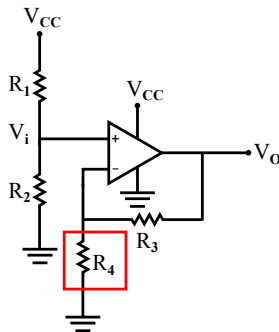
## Question 8

- \* (c) Design (by using the non-inverting amplifier circuit) a circuit such that the output voltage ( $V_o$ ) is directly proportional to the input force ( $F$ ).





## Question 8

- \* (d) The system requires that
  - \* when the force  $F = 0N$ , the output voltage  $V_o = 4V$
  - \* when  $F = 20N$ ,  $V_o = 12V$
  - \* Construct the circuit designed in (c) using only one FSR, one op-amp, one  $12V$  power supply, and an unlimited number of  $1k\Omega$  resistors.


## Question 8

- \* (e) Using the above circuit, what is the value of  $V_o$  when someone hits the hammer too hard, generating a force of  $200N$ ?
- \* (f) Suggest modification(s) to your answer in Part (d) such that the maximum allowable force to the circuit is  $60N$ . You can only use the available components in Part(d), while maintaining  $V_o$  to be directly proportional to  $F$ .

## Appendix(Question 9)


- \* Fill in the values of  $R_1$  and  $R_2$  required to satisfy the equations in the left column of the following table. The values must be non-negative (i.e., in the range  $[0, \infty]$ )

	$R_1$	$R_2$
$V_0 = 2V_2 - 2V_1$		
$V_0 = V_2 - V_1$		
$V_0 = 4V_2 - 2V_1$		

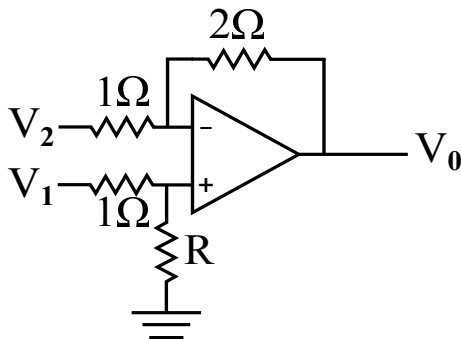

## Appendix(Question 10)


\* What is  $V_o$ ?

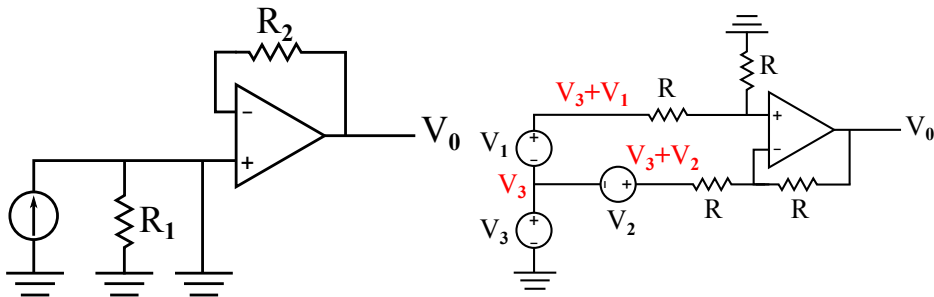


## Appendix(Question 11)

- \* Students **Jody**, **Chris**, **Pat**, **Kim** and **Leon** are trying to design a controller for a display of three robotic mice in the Rube Goldberg Machine, using a  $10V$  power supply and three motors.
  - \* The first is supposed to spin as fast as possible (in one direction only), the second at half of the speed of the first, and the third at half of the speed of the second.
  - \* Assume the motors have a resistance of approximately  $5\Omega$  and that rotational speed is proportional to voltage.
- \* For each design, indicate the voltage across each of the motors.


## Appendix(Question 11 – Jody's Design)

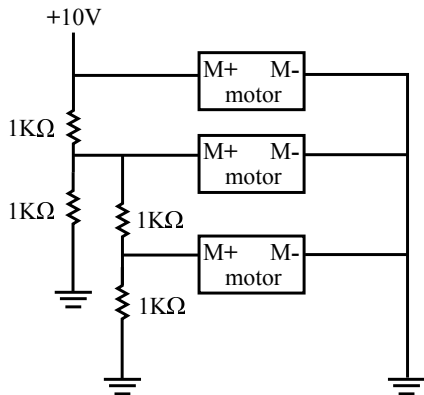
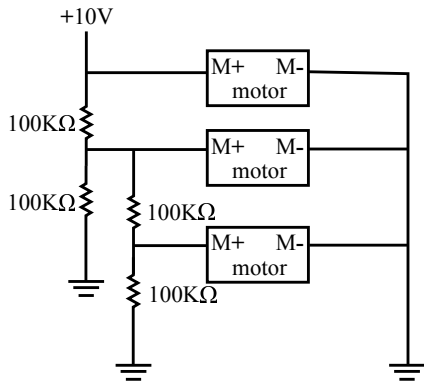
## Appendix(Question 11 – Chris's Design)




## Appendix(Question 11 – Pat's Design)

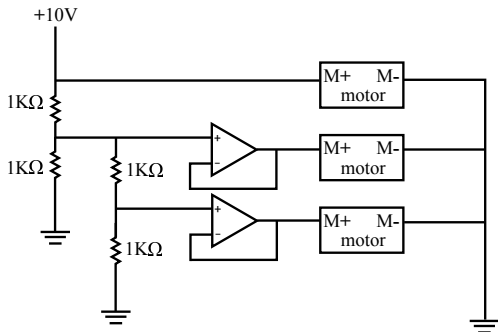



## Appendix(Question 11 – Kim's Design)

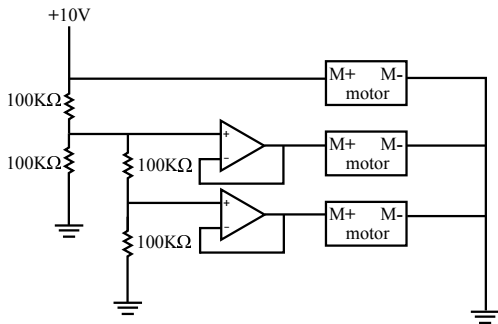

## Appendix(Question 11 – Leon's Design)

